

2017

(CBCS)

(2nd Semester)

ELECTRONICS

SECOND PAPER

(Semiconductor Physics)

Full Marks :75

Time : 3 hours

(PART : A - OBJECTIVE)

(Marks:25)

The figures in the margin indicate full marks for the questions

SECTION – A

(Marks:10)

Put a Tick (✓) mark against the correct answer in the brackets provided for it : 1×10 =10

1. Silicon has $Z = 14$. Its outermost orbit is
(a) partially filled () (b) half-filled ()
(c) completely occupied () (d) empty ()
2. Addition of impurity to a pure semiconductor is called
(a) rectification () (b) drift current ()
(c) doping () (d) extrinsic semiconductor ()
3. The knee voltage of a diode is approximately equal to
(a) applied voltage () (b) breakdown voltage ()
(c) forward voltage () (d) barrier potential ()
4. The ripple factor of a full-wave rectifier is
(a) 2 () (b) 1.21 ()
(c) 2.5 () (d) 0.48 ()
5. When used in a circuit, Zener diode is always
(a) forward biased () (b) connected in series ()
(c) reversed biased () (d) overheated ()
6. A semiconductor device that resembles a voltage variable capacitor is known as
(a) tunnel diode () (b) varactor diode ()
(c) Schottky diode () (d) PIN diode ()

(2)

7. The operating point of a transistor is also called
(a) quiescent point () (b) cut-off point ()
(c) saturation point () (d) intersection point ()
8. The output impedance of a transistor is
(a) low () (b) high ()
(c) very low () (d) zero ()
9. The maximum distortion is found in
(a) class A amplifier () (b) class B amplifier ()
(c) class C amplifier () (d) class AB amplifier ()
10. A transistor converts
(a) d.c. power to a.c. power ()
(b) a.c. power to d.c. power ()
(c) high resistance to low resistance ()
(d) low resistance to high resistance ()

SECTION – B
(Marks: 15)

Answer the following questions:

3 × 5=15

1. Explain formation of depletion region in a $p-n$ junction.

Or

Explain the capacitive effects of junction diode.

2. A crystal diode having internal resistance $r_f = 20 \Omega$ is used for half-wave rectification. If the applied voltage $V = 50 \sin \omega t$ and load resistance $R_L = 800 \Omega$, find the efficiency of rectification.

Or

What are the advantages of full-wave rectification over half-wave rectification.

3. Explain how Zener diode can be used as a peak clipper.

Or

What are the advantages of PIN diode over $p-n$ junction diode?

4. What is transistor? Write the symbols of $p-n-p$ and $n-p-n$ transistors.

Or

What is thermal runaway? How will you avoid this in a transistor?

5. Explain bandwidth of an amplifier with necessary diagram.

Or

Draw a frequency response curve for RC coupled transistor amplifier.

(3)

(PART: B – DESCRIPTIVE)

(Marks: 50)

The figures in the margin indicate full marks for the questions

1. (a) Describe with a diagram the atomic model proposed by Niels Bohr. What do you mean by valence electrons? 3+1 = 4
- (b) What is energy band? Classify solids in terms of energy band. 1+3=4
- (c) Determine the electronic distribution of xenon atom having $Z = 54$. 2

Or

2. (a) What are intrinsic and extrinsic semiconductors? How is p -type of extrinsic semiconductors formed? 2+3=5
- (b) Explain the V - I characteristics of P - N junction diode with suitable diagrams. 4
- (c) What is Zener breakdown? 1
3. (a) What do you understand by the d.c. and a.c. resistances of a semiconductor diode? How will you determine them? 2+3=5
- (b) Explain with a diagram how semiconductor diode can be used as a full-wave rectifier. Show that its maximum efficiency is 81.2%. 2+3= 5

Or

4. (a) What is ripple factor? Derive the value of ripple factor for half-wave rectifier. 1+3= 4
- (b) Describe the filtering action of capacitor-input filter. 2
- (c) Explain different equivalent circuits of a semiconductor diode. 4
5. (a) What is Zener diode? Explain how Zener diode maintains constant voltage across the load. 1+3=4
- (b) What is tunneling effect? Explain the V - I characteristics of tunnel diode. Mention some important applications of tunnel diode. 1+3+2=6

Or

6. (a) Describe the construction, resistance curve and applications of thermistor. 2+2+2=6
- (b) What is photodiode? How is current reduced to zero in photodiode? 2+2=4
7. (a) What is meant by transistor biasing? What are the essentials of the transistor biasing circuit? 1+3=4
- (b) Explain with a diagram, the input characteristics of a CE transistor. State the advantages of a CE mode over other mode of operations. 3+3=6

(4)

Or

8. (a) Show that $\beta = \frac{\alpha}{1 - \alpha}$

where the symbols have their usual meanings. 3

(b) Explain with a diagram the leakage current in CB circuit of a transistor. 3

(c) Discuss the transistor action in *n-p-n* mode with a diagram. 4

9. (a) Explain how transistor can be used as an amplifier. What do you mean by operating point of a transistor circuit? 3+1=4

(b) Describe class A, class B, class C, and class AB amplifiers. Illustrate your answer with suitable diagrams. 6

Or

10.(a) Explain in brief the frequency response curve of an amplifier. What do you mean by resonant frequency? 3+1=4

(b) Write down the steps for construction of d.c. load line. Also explain the terms 'cut-off point' and 'saturation point'. 3+2=5

(c) Define bandwidth of an amplifier. 1

★ ★ ★