

2 0 1 9

(CBCS)

(2nd Semester)

ELECTRONICS

SECOND PAPER

(Semiconductor Physics)

Full Marks : 75

Time : 3 hours

(PART : A—OBJECTIVE)

(*Marks : 25*)

The figures in the margin indicate full marks for the questions

SECTION—A

(*Marks : 10*)

Tick (✓) the correct answer in the brackets provided :

1×10=10

1. The leakage current across a $p-n$ junction is due to

(a) minority carriers ()

(b) majority carriers ()

(c) junction capacitance ()

(d) impurity ()

2. In a semiconductor, the energy gap between valence and conduction bands is about

(a) 15 eV ()

(b) 10 eV ()

(c) 5 eV ()

(d) 1 eV ()

3. The primary function of a filter is to

(a) minimize a.c. input variations ()

(b) suppress odd harmonics in the rectifier output ()

(c) stabilize d.c. level of the output voltage ()

(d) remove ripples from the rectified output ()

4. An ideal crystal diode is one which behaves as a perfect _____ when forward biased.

(a) conductor ()

(b) insulator ()

(c) resistance material ()

(d) capacitance material ()

5. Zener diodes are used primarily as

(a) amplifiers ()

(b) voltage regulators ()

(c) rectifiers ()

(d) oscillators ()

6. The device associated with voltage-controlled capacitance is

(a) LED ()

(b) photodiode ()

(c) varactor diode ()

(d) zener diode ()

7. In a *p-n-p* transistor, the current carriers are

(a) acceptor ions ()

(b) donor ions ()

(c) free electrons ()

(d) holes ()

8. The element that has the biggest size in a transistor is

(a) collector ()

(b) base ()

(c) emitter ()

(d) collector-base junction ()

9. The lower and upper cut-off frequencies of transistor amplifier are also called

(a) sideband frequencies ()

(b) resonant frequencies ()

(c) half-resonant frequencies ()

(d) half-power frequencies ()

10. The d.c. load line of a transistor circuit

(a) has a negative slope ()

(b) is a curved line ()

(c) gives graphic relation between I_C and I_B ()

(d) does not contain the Q-point ()

SECTION—B

(Marks : 15)

Answer the following questions :

3×5=15

1. What do you mean by a hole in a semiconductor? Discuss the formation of hole current.

OR

Explain the capacitive effects of junction capacitance.

2. What are the important electrical properties of a capacitor and an inductor in making a filter circuit?

OR

Compare half-wave and full-wave bridge rectifiers.

3. Explain the working of a Zener diode as peak clipper.

OR

Describe the construction of thermistor.

4. What is thermal runaway? How will you avoid this in a transistor?

OR

A transistor has $\beta = 98$, $I_B = 100 \text{ A}$ and $I_{CO} = 6 \text{ A}$. Calculate I_C and I_E .

5. Explain frequency response curve and bandwidth of an amplifier with necessary diagram.

OR

Explain how a transistor acts as an amplifier.

(PART : B—DESCRIPTIVE)

(Marks : 50)

The figures in the margin indicate full marks for the questions

1. (a) Discuss the behaviour of a $p-n$ junction under forward and reverse biasing. 2+2=4
- (b) Explain the salient features of Bohr's atomic model. 4
- (c) Which are the most commonly used semiconductors and why? 2

OR

2. (a) What is a $p-n$ junction? Explain the formation of potential barrier in a $p-n$ junction. 1+2=3
- (b) What are intrinsic and extrinsic semiconductors? How is p -type of extrinsic semiconductors formed? 2+2=4
- (c) Give the energy band description of conductors, semiconductors and insulators. 3
3. (a) Explain with a diagram, how semiconductor diode can be used as a full-wave rectifier. Show that its maximum efficiency is 81.2%. 2+3=5
- (b) What do you understand by d.c. and a.c. resistances of a semiconductor diode? 2
- (c) Describe the filtering action of a capacitor filter. 3

OR

4. (a) Show that the value of ripple factor for half-wave rectifier is 1.21. 2
- (b) Explain approximate equivalent circuit of semiconductor diode. 2
- (c) Describe the filtering action of π -filter. 3

(d) A full-wave rectifier uses two diodes, the internal resistance of each diode may be assumed constant at 20Ω . The transformer r.m.s. secondary voltage from centre tap to each end of secondary is 50 V and load resistance is 980Ω . Find—(i) the mean load current and (ii) the r.m.s. value of load current. 3

5. (a) Explain the operation and characteristics of a photodiode. 2+2=4
 (b) Describe the operation and applications of Schottky diode. 3
 (c) Explain the working of a tunnel diode oscillator. 3

OR

6. (a) Describe the operation and diode resistance of a PIN diode. 3
 (b) Explain any three applications of varactor diode. 3
 (c) What is tunnelling effect? Explain the $V-I$ characteristics of tunnel diode. 1+3=4
7. (a) With diagram, discuss the working of $n-p-n$ transistor. 3
 (b) Define β and β_1 of a transistor. Show the relation $\beta = \frac{\beta_1}{1 - \beta_1}$, where the symbols have their usual meanings. 2+3=5
 (c) What is meant by transistor biasing? What are the important biasing rules? 1+1=2

OR

8. (a) Explain with diagram, the input and output characteristics of CE configuration in an $n-p-n$ transistor. 5
 (b) With diagram, explain the three primary currents which flow in a properly-biased $p-n-p$ transistor. 3
 (c) In CB connection, $\beta_{CB} = 0.9$. If the emitter current is 1 mA , determine the value of base current. 2

9. (a) Explain the terms input resistance, output resistance, current gain, voltage gain and power gain of a transistor amplifier. 5
- (b) For a single-stage transistor amplifier, the collector load is $R_C = 2\text{ k}$ and the input resistance $R_i = 1\text{ k}$. If the current gain is 50, calculate the voltage gain of the amplifier. 2
- (c) Using the output characteristics along with the d.c. load line of CE transistor circuit, explain the terms cut-off, saturation and active region. 3

OR

10. (a) Describe class-A, class-B, class-C and class-AB amplifiers. 4
- (b) A change of 200 mV in base-emitter voltage causes a change of 100 A in the base current. Find the input resistance of the transistor. 2
- (c) How will you draw d.c. load line on the output characteristics of a transistor? What is its importance? 2+2=4
